

Lab 1: Logic Gates and Multiplexer_4_1

Today we will get introduced to Vivado and the general flow of designing digital circuits with VHDL. We will see how to create a Vivado project, how to create VHDL entities, and how to test the entities in simulation.

14:15-14:35: Demonstration 1 – AND-gate

1. Introduction to Vivado
2. Creation of a project
3. Creation of our first VHDL entity: The AND-gate
4. Testing of the entity in behavioral simulation

a	b	o
0	0	0
0	1	0
1	0	0
1	1	1

Table 1: AND-gate truth table

14:35-15:00: Task 1 – OR-gate and NOT-gate

1. In the same project, create a new file 'or_gate.vhd'
 - a. Two *STD_LOGIC* inputs *a* and *b*, one *STD_LOGIC* output *o*
2. Write VHDL such that the relationship between inputs *a* and *b* and output *o* follows the truth table in table 2
3. Test your design in behavioral simulation
4. Repeat for 'not_gate.vhd', truth table in table 3

a	b	o
0	0	0
0	1	1
1	0	1
1	1	1

Table 2: OR-gate truth table

a	o
0	1
1	0

Table 3: NOT-gate truth table

15:00-15:05: Break

15:05-15:15: Demonstration 2 – Vivado Block Design

1. Creation of new block design
2. Block design of truth table in table 4
3. Behavioral simulation of block design

15:15-15:45: Task 2 – Multiplexer_4_1

1. Create a new block design 'multiplexer_4_1'
2. Using only AND-gates, OR-gates, and NOT-gates, implement a 4x1 multiplexer, figure 1 and table 5, in block design
3. Verify the behavior in simulation
4. Hint will be given if required

a	b	c	o
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table 4

Bonus Task

- Implement a 2x1 multiplexer in a new VHDL file (that is, write the multiplexer fully as a new VHDL entity and not in block design)
- Can you make it as *generic* as possible, so the size of the multiplexer is easily changeable? 2x1, 4x1, 4x2, etc. Think about which parameters you would need in order to make the multiplexer generic in size.

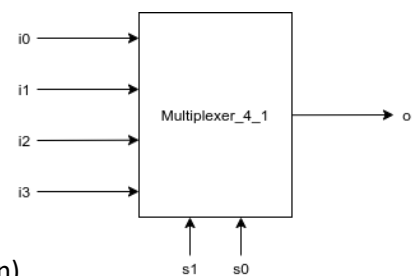


Figure 1: 4x1 multiplexer

s1	s0	o
0	0	i0
0	1	i1
1	0	i2
1	1	i3

Table 5: 4x1 multiplexer truth table