

# ***ELE-plan for i dag***

## ***Forstærker med negativ feedback***

- *Systematisere fejl - i forhold til ideel performance*

## ***Modkoblet forstærker***

- *Princip med  $\alpha$  og  $\beta$*
- *$A_{OL}$ 's indflydelse på lukketsløjfeforstærkningen  $A_{CL}$*
- *Fejlfaktor  $K_f$*

*Pause*

## ***Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$***

- *Ikke-inverterende kobling som eksempel*

*Pause*


## ***Generelle betragtninger af forstærker med negativ feedback***

- *Indgående forstærkninger*
- *Feedback typer*
- *Baggrund for valg af feedback type (set fra kilde/belastning)*
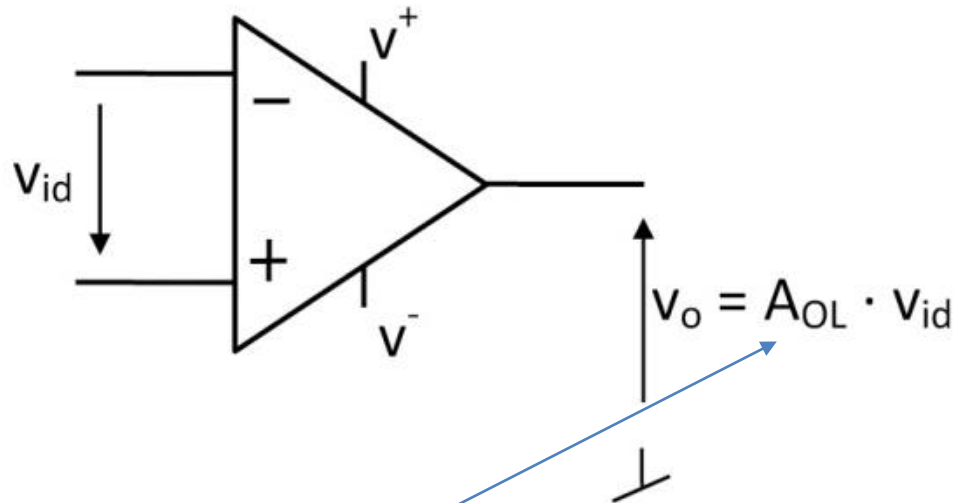
## ***Forberedelse til lektion 2***

Man kommer langt med Kirchhoff's og Ohm's love, men skal man foretage et ***systematiseret design*** og i denne forbindelse kunne foretage ***kvalificerede komponentvalg***, så er man nødt til ligeledes at kunne ***systematisere sine fejlberegninger***.


Anvender man Op Amps i sin signalbehandling, kan man med fordel **relatere de aktuelle egenskaber til den ideelle performance** – vurdere hvilke størrelser, der giver anledning til hvilke fejl og måske sætte en kvantitativ størrelse på disse.




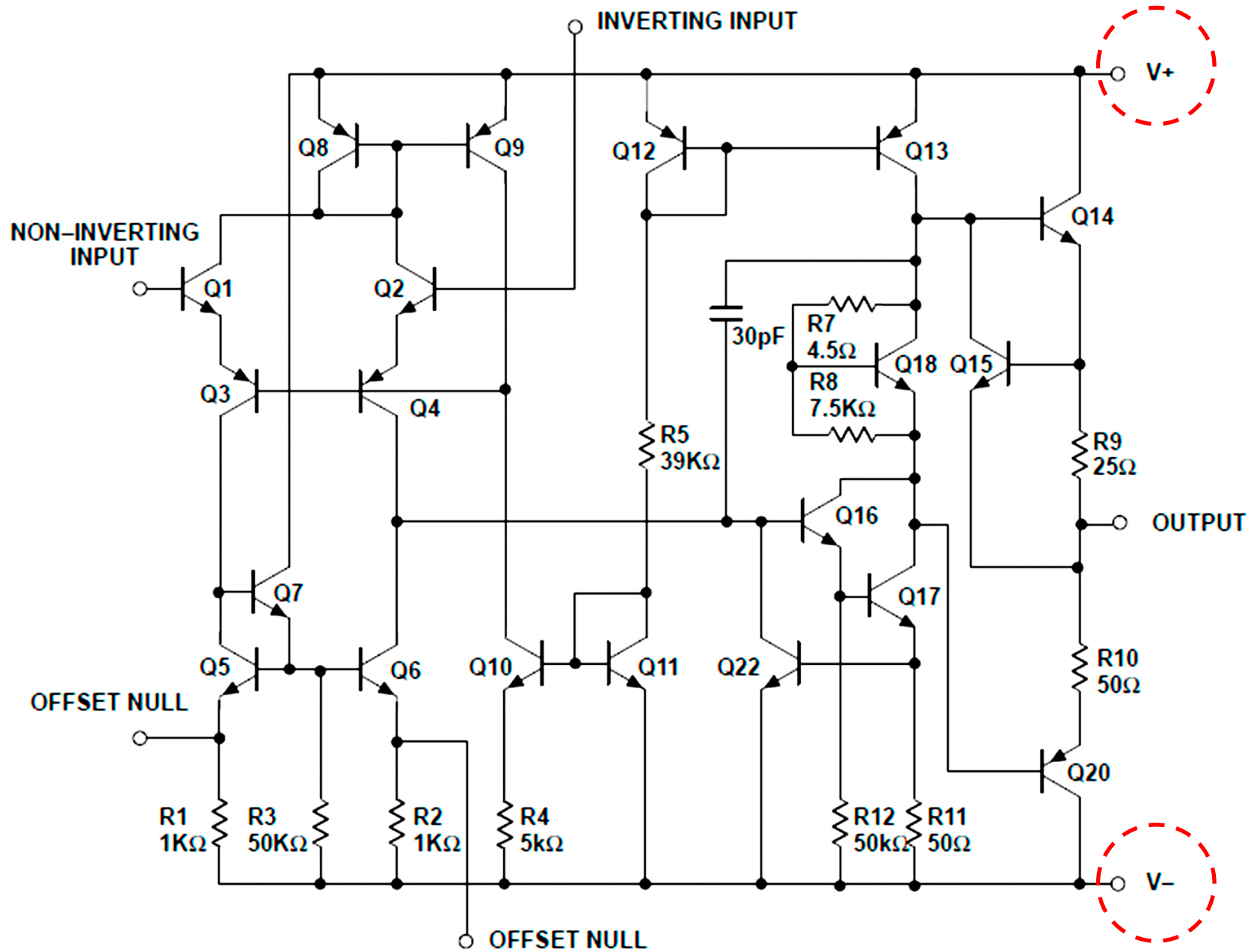**"Open Loop Gain"**

Åbensløjfeforstærkning - forstærkning **uden** feedback


Hvordan ser overføringsfunktionen  $v_o$  som funktion af  $v_{id}$  ud?  
Ideelt? I praksis?



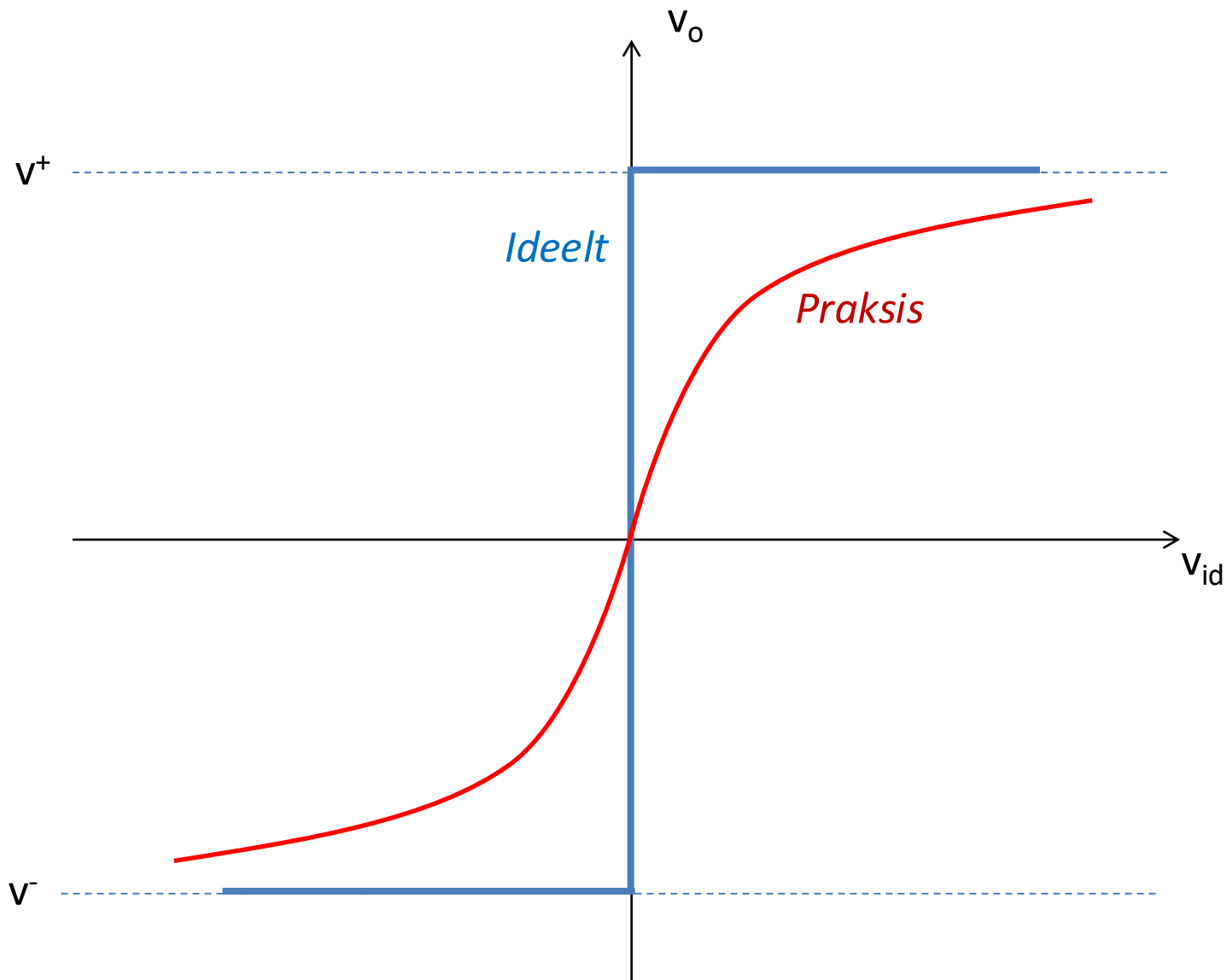


$$v_o = A_{OL} \cdot v_{id} \quad \Rightarrow \quad \frac{dv_o}{dv_{id}} = A_{OL}$$

# *Modkoblet forstærker*

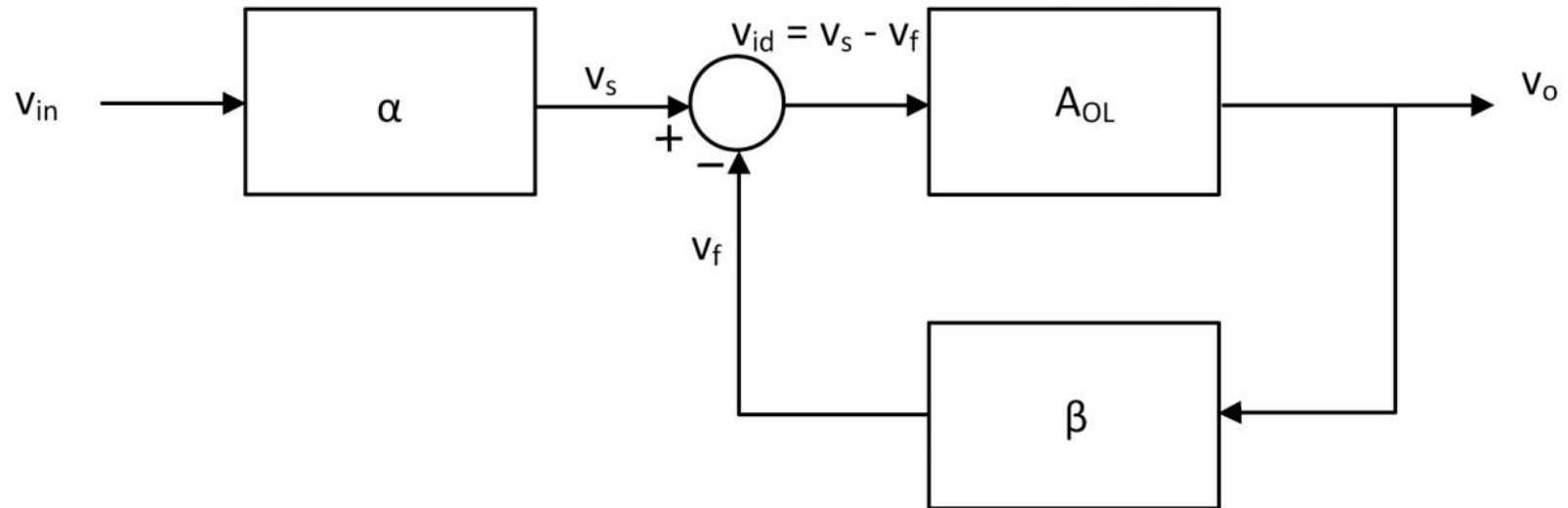

*Note: Forstærker med negativ feedback*


# *Inverterende forstærker*

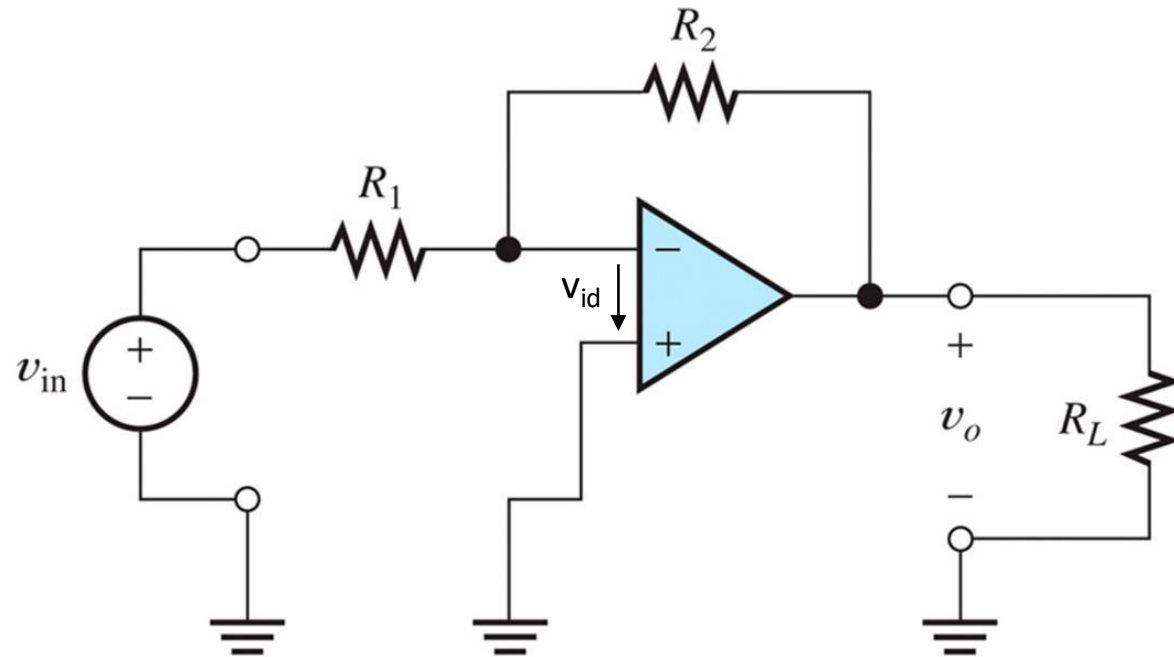

$$\alpha = ?$$

$$\beta = ?$$

# *Ikke-inverterende forstærker*

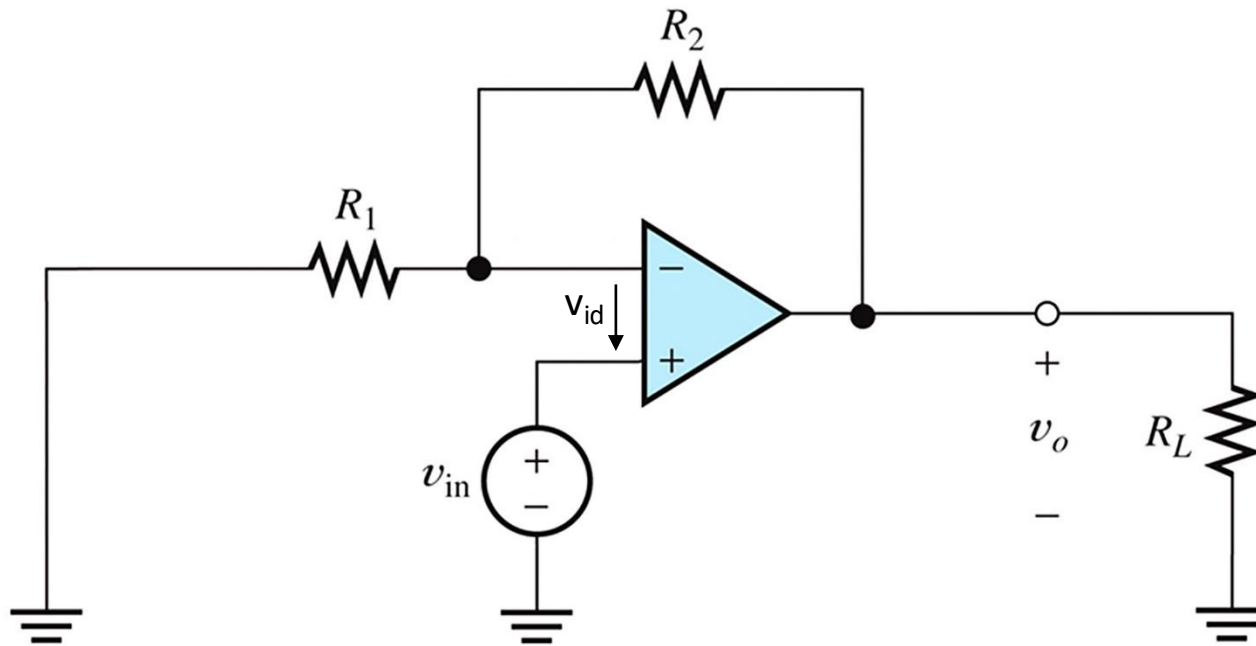


$$\alpha = ?$$

$$\beta = ?$$




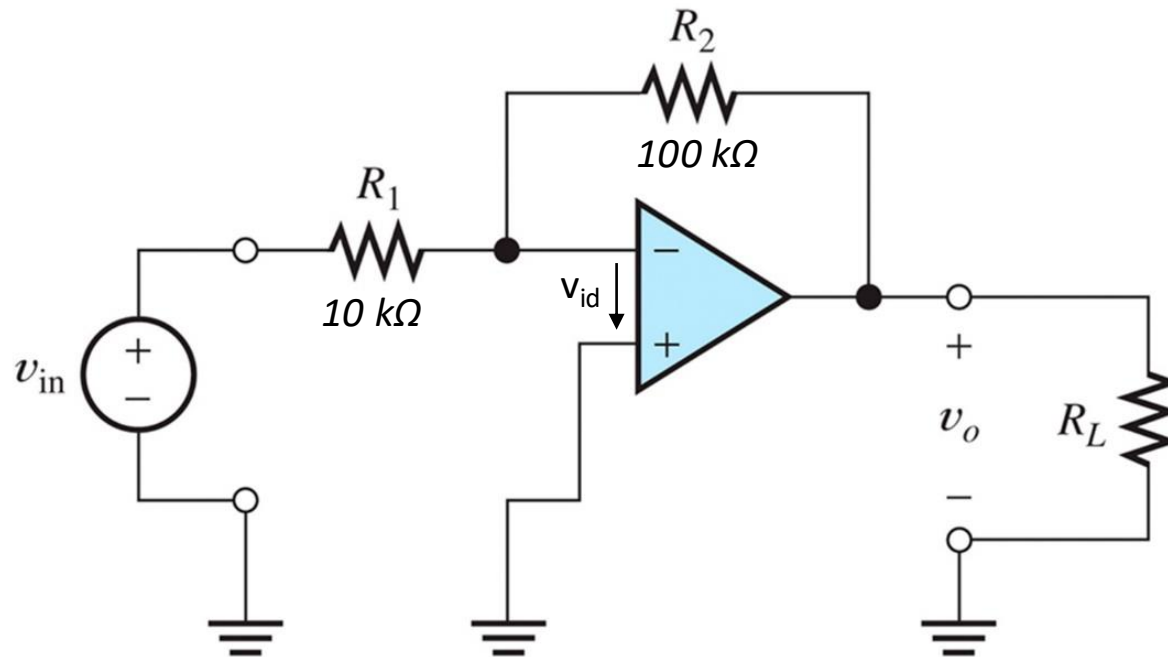**Sp. 3 fra forberedelsen:**


En inverterende forstærker som på figur 2.5 er bygget med  $R_1 = 10 \text{ k}\Omega$  og  $R_2 = 100 \text{ k}\Omega$ .  $A_{OL}$  er  $10^6$ . Hvor stor er afvigelsen fra den ideelle forstærkning?



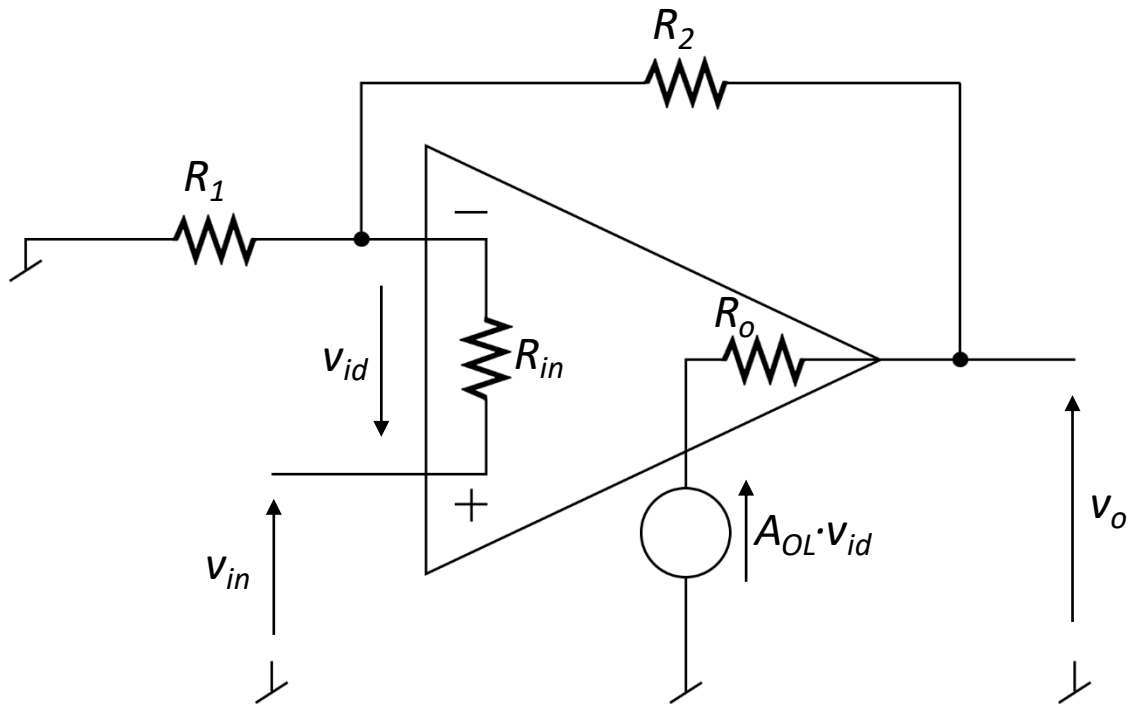
*Effekt af negativ feedback på  $Z_o$ ,  $Z_{in}$  og  $A_{CL}$*


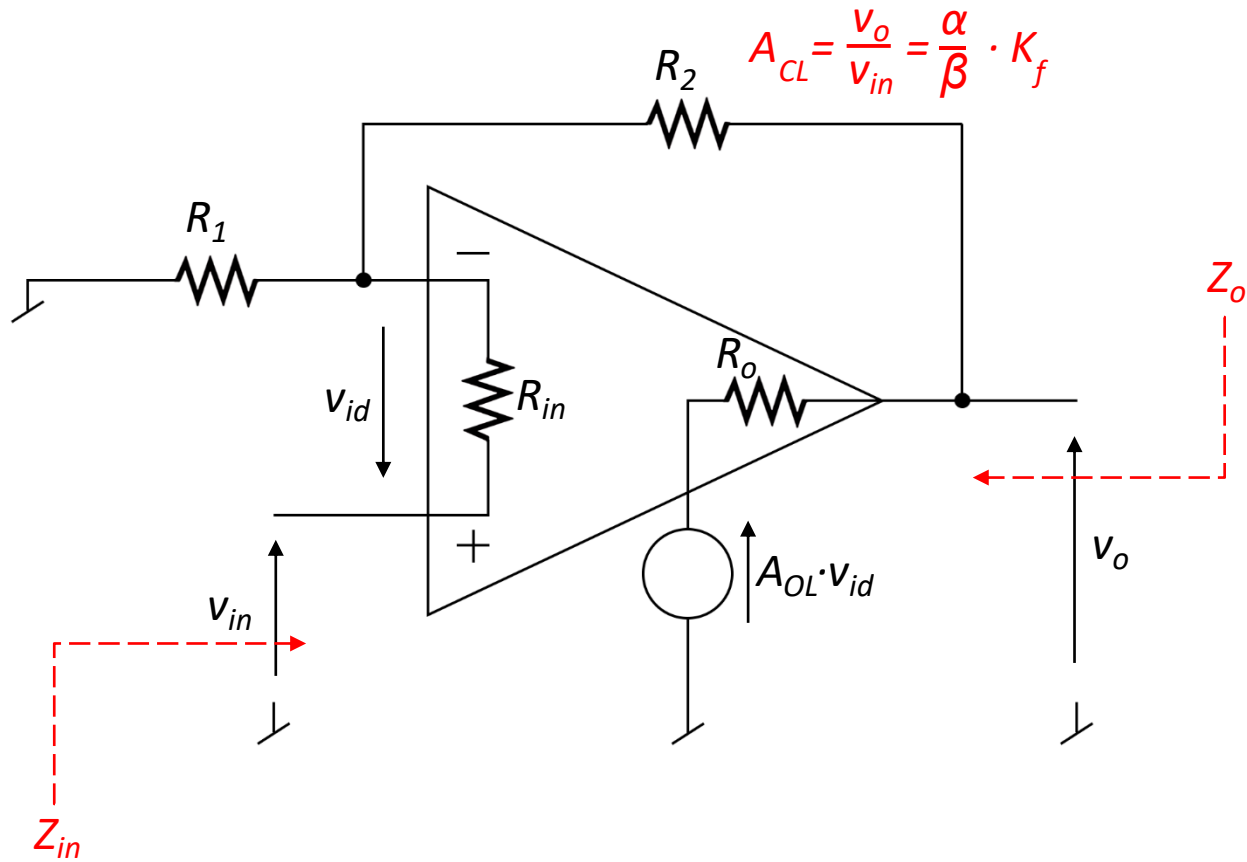
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$



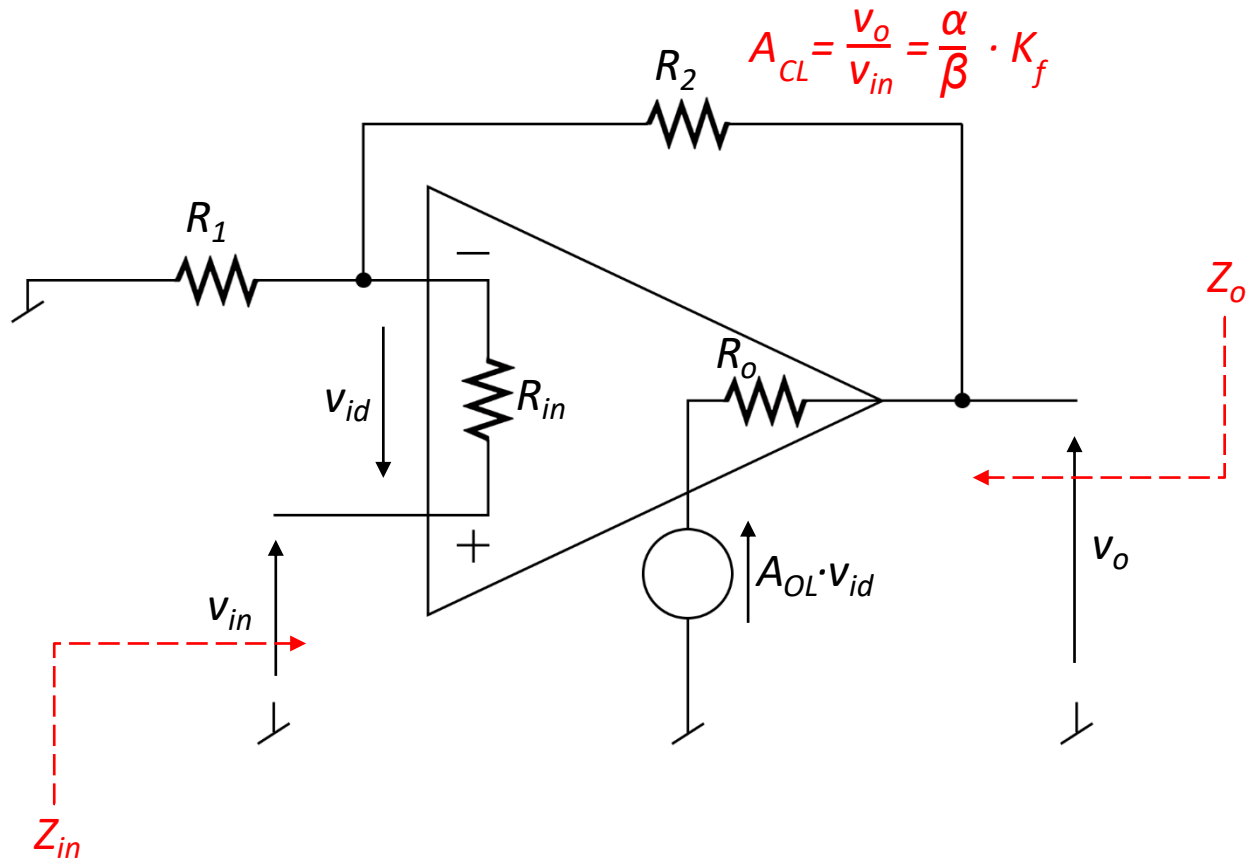
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$



Ideal Op Amp:

$A_{OL}$	$\rightarrow$	$\infty$
$R_{in}$	$\rightarrow$	$\infty$
$R_o$	$\rightarrow$	$0 \Omega$

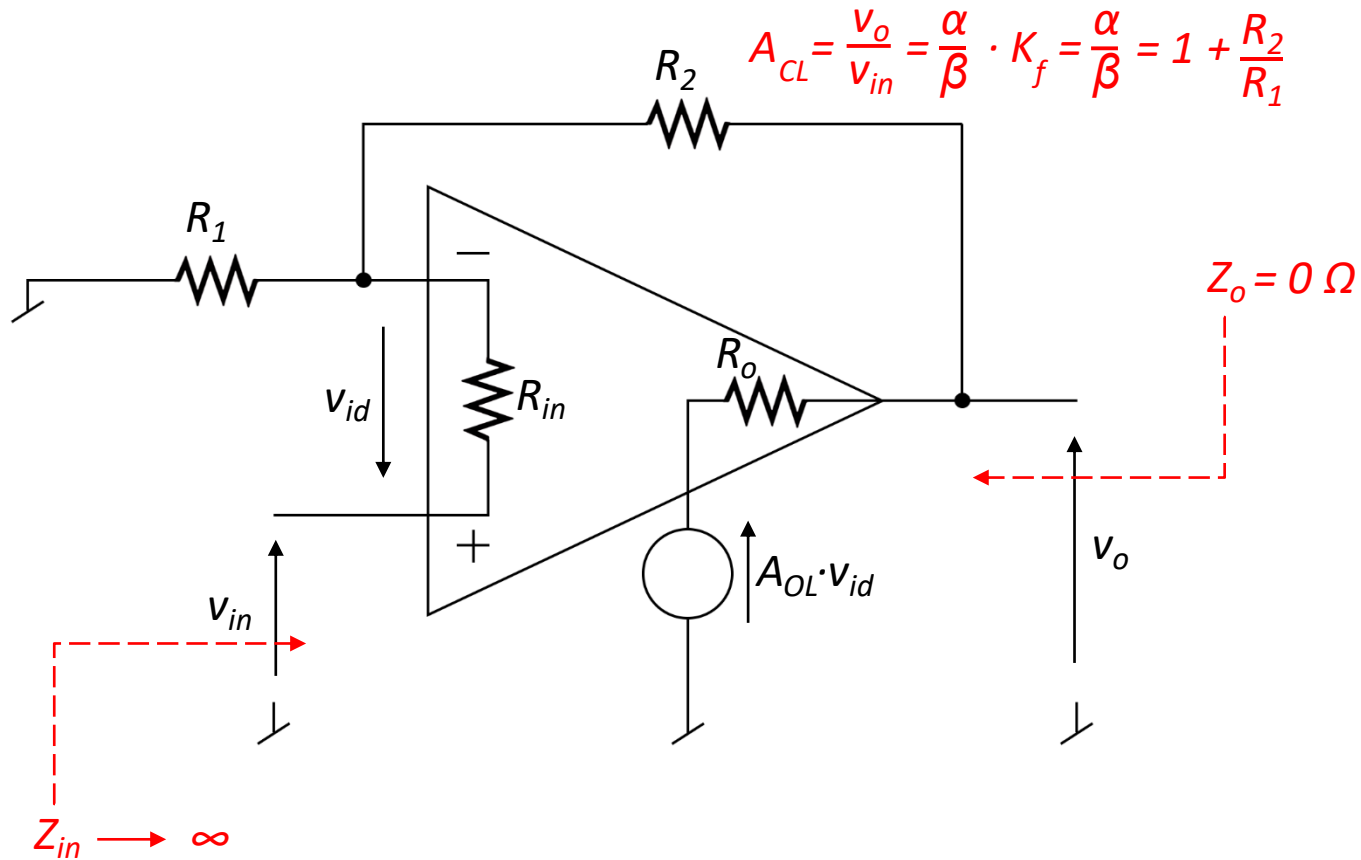
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$



Ideel Op Amp:

$A_{OL}$	$\rightarrow$	$\infty$
$R_{in}$	$\rightarrow$	$\infty$
$R_o$	$\rightarrow$	$0 \Omega$
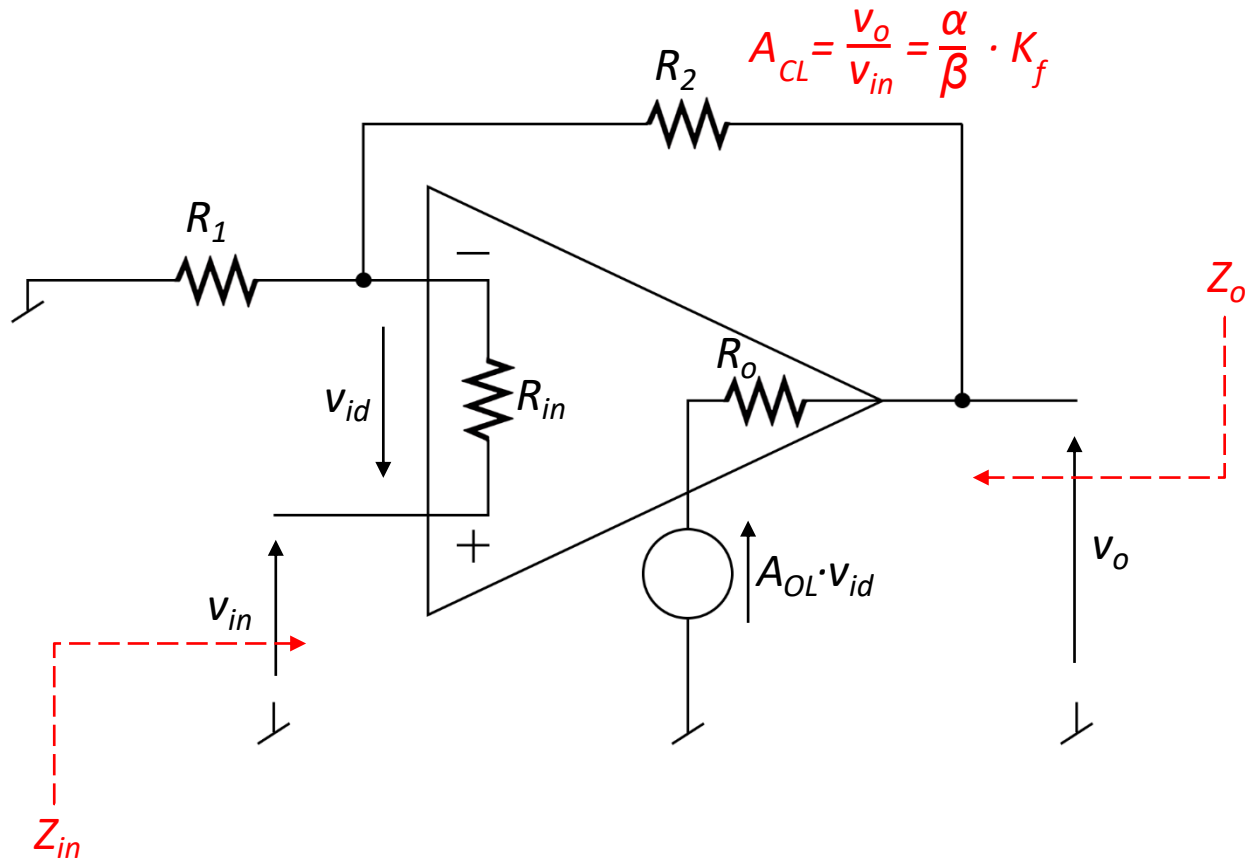
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$




**Ikke ideel Op Amp:**

$A_{OL}$	$\neq$	$\infty$
$R_{in}$	$\neq$	$\infty$
$R_o$	$\neq$	$0 \Omega$

Se datablad for  $\mu A741$
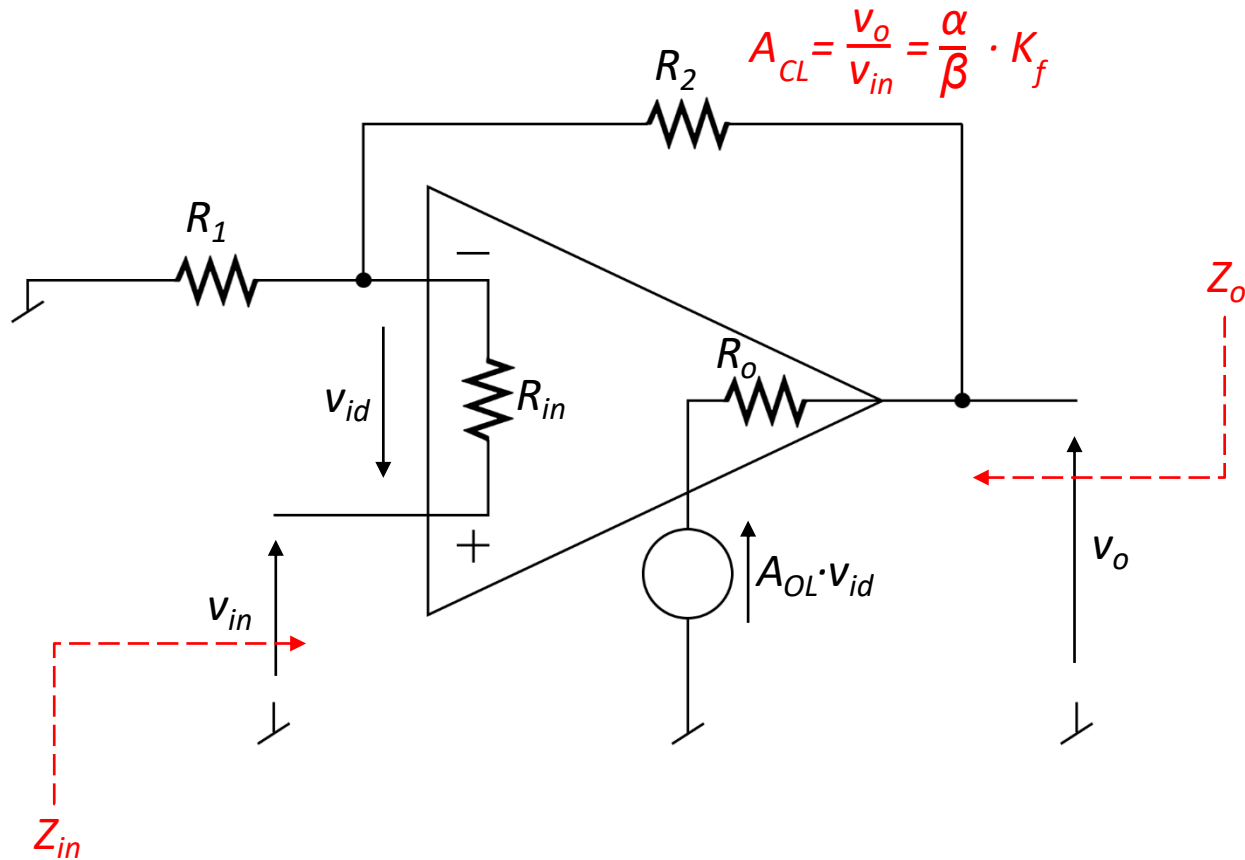
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$




**Ikke ideel Op Amp:**

$A_{OL}$	$\neq$	$\infty$
$R_{in}$	$\neq$	$\infty$
$R_o$	$\neq$	$0 \Omega$


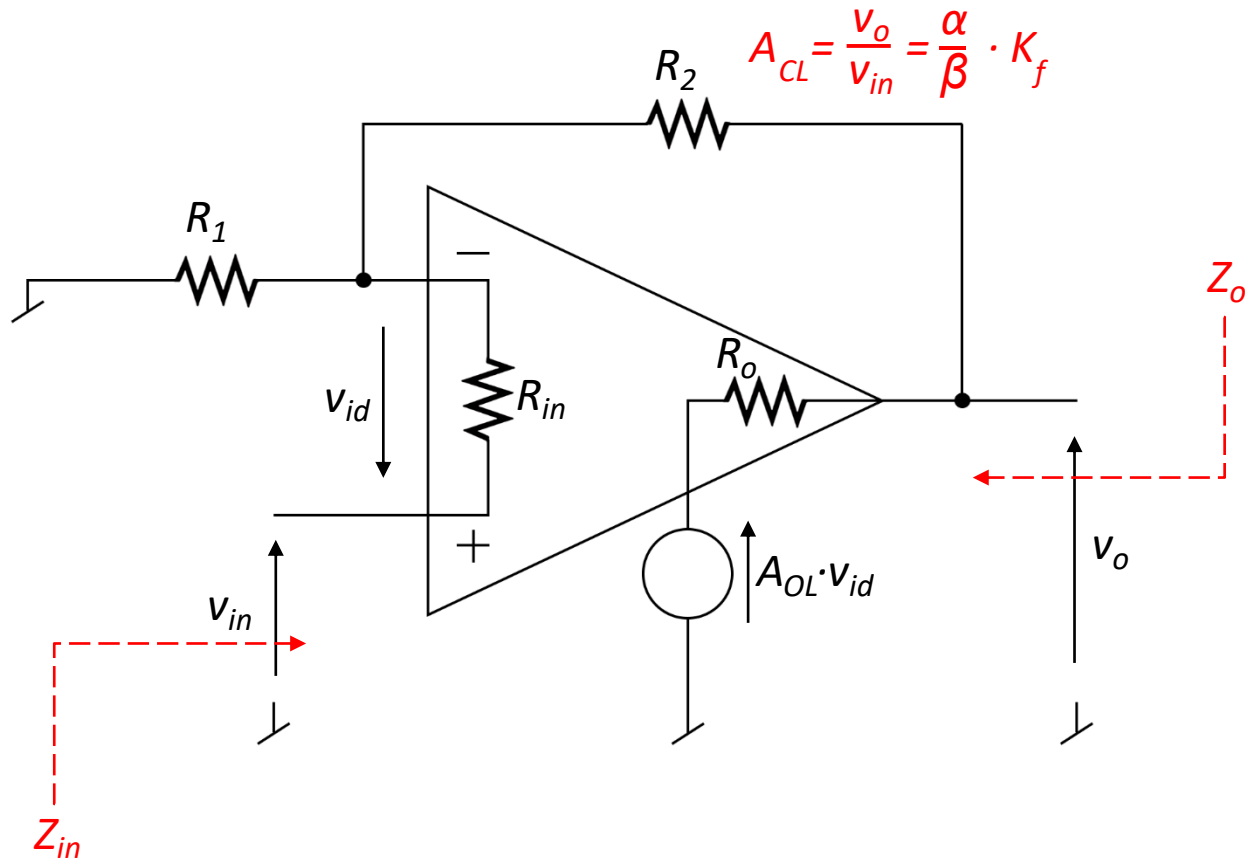
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$




**Ikke ideel Op Amp:**

$A_{OL}$	$\neq$	$\infty$
$R_{in}$	$\neq$	$\infty$
$R_o$	$\neq$	$0 \Omega$


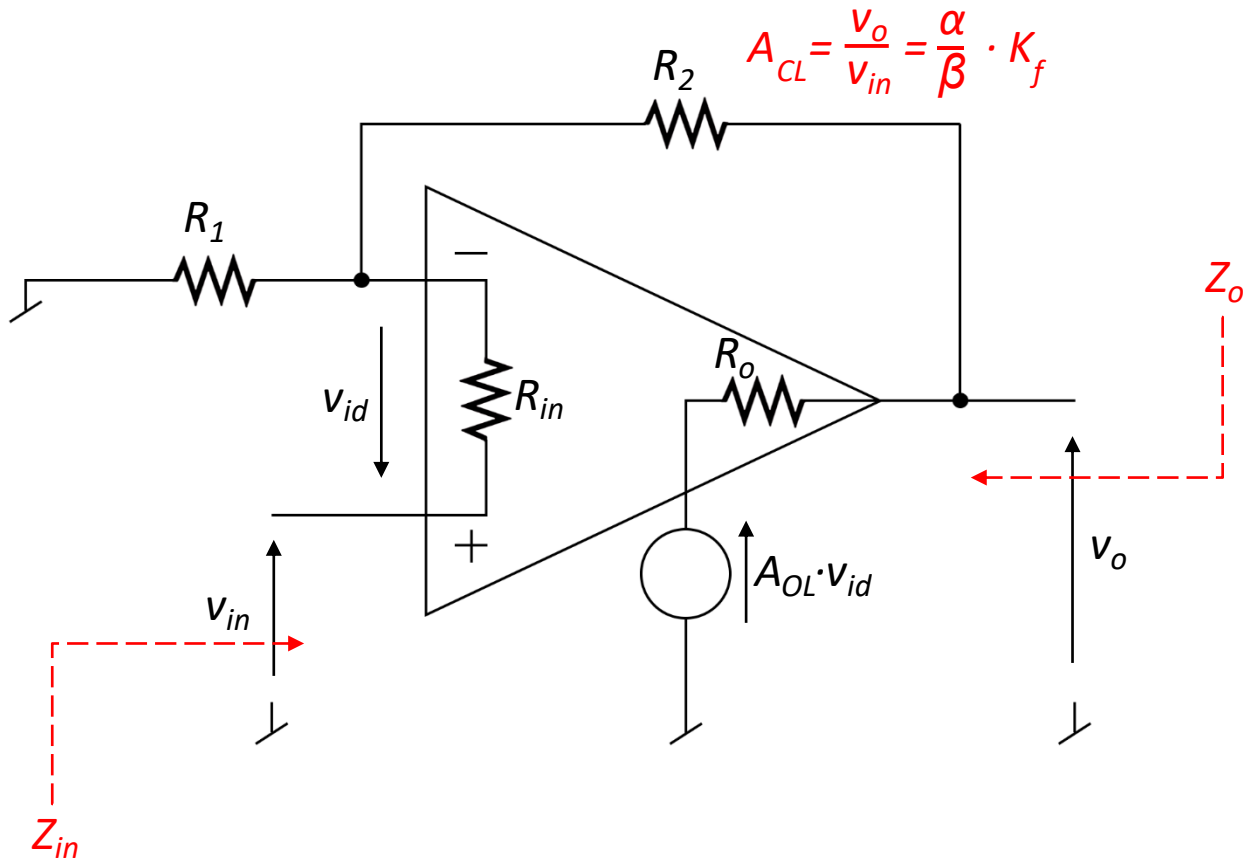
# Effekt af negativ feedback på $Z_o$ , $Z_{in}$ og $A_{CL}$



**Ikke ideel Op Amp:**


$A_{OL}$	$\neq$	$\infty$
$R_{in}$	$\neq$	$\infty$
$R_o$	$\neq$	$0 \Omega$




Vi starter lige med at beregne  $\beta$

*Generelle betragtninger af forstærker med negativ feedback*


# Forstærker med negativ feedback

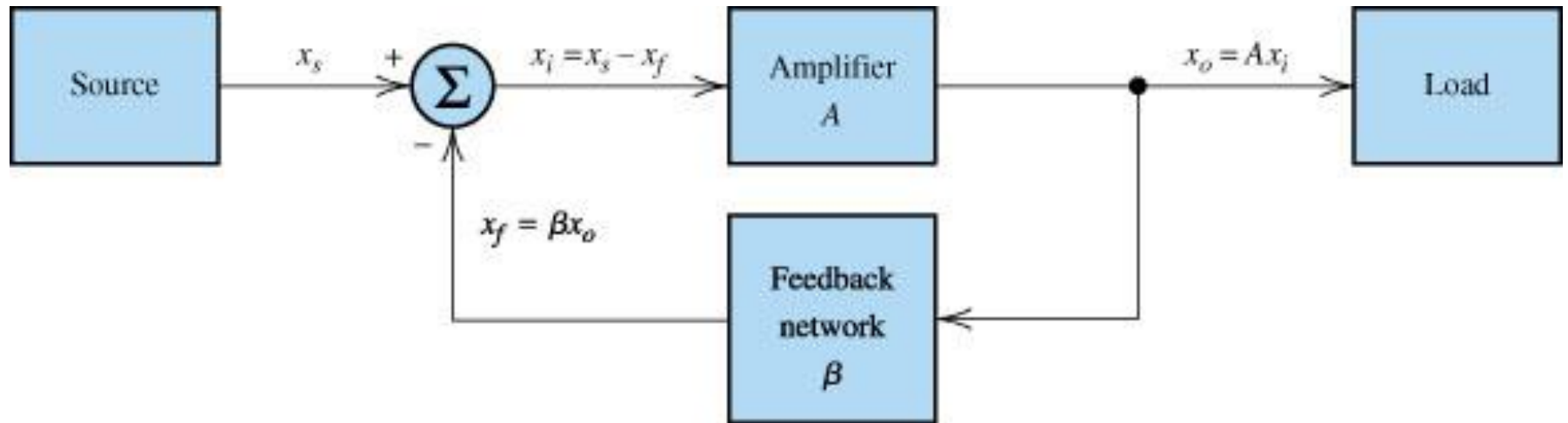


Figur 9.1

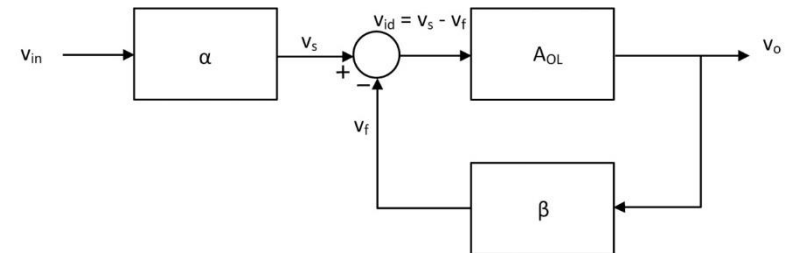

# Forstærker med negativ feedback

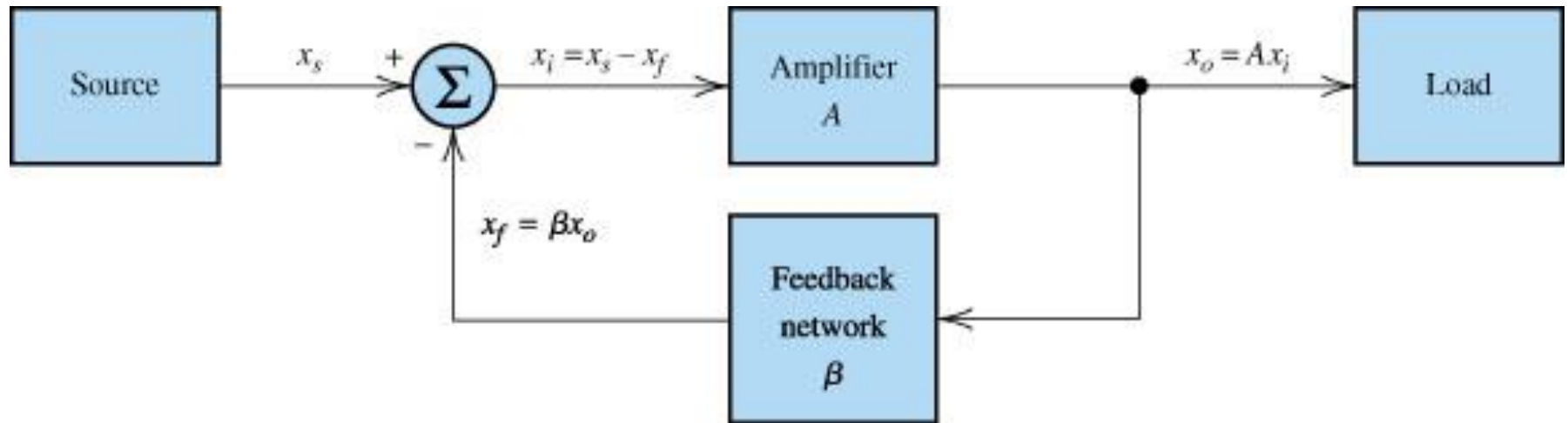


Figur 9.1

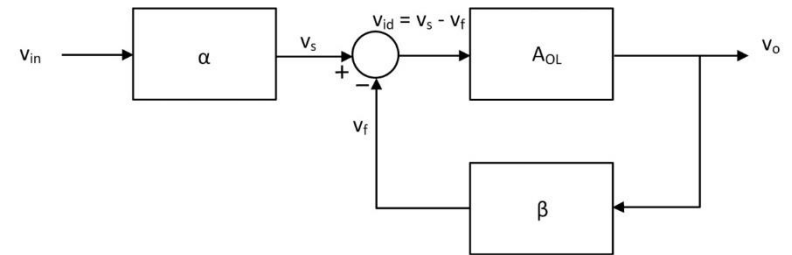


$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \left. \frac{1}{\beta} \right|_{\beta A \rightarrow \infty}$$

# Forstærker med negativ feedback

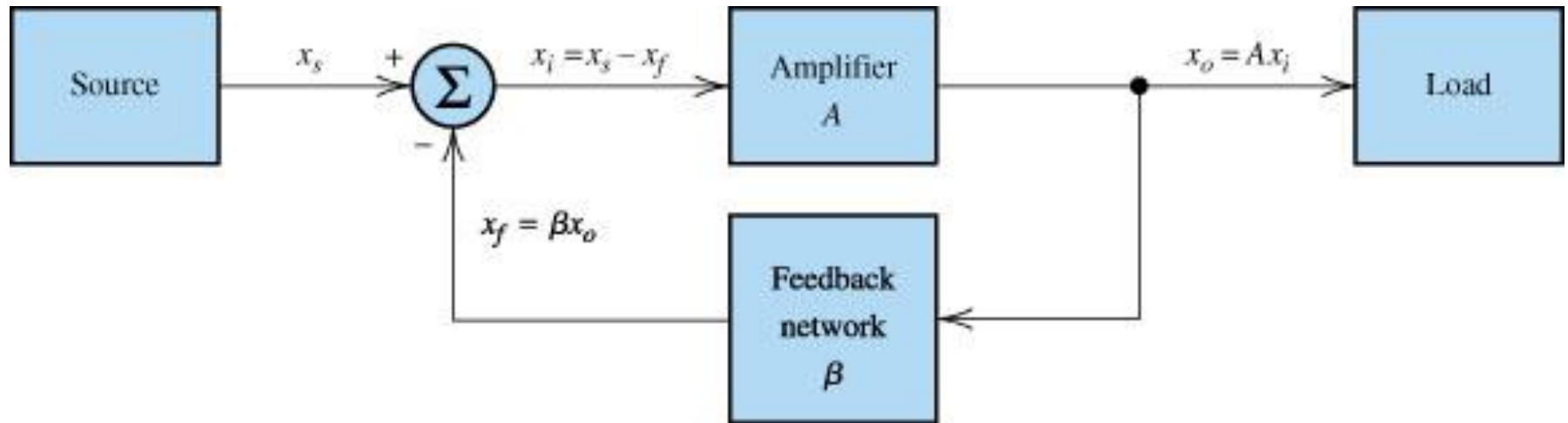


Figur 9.1

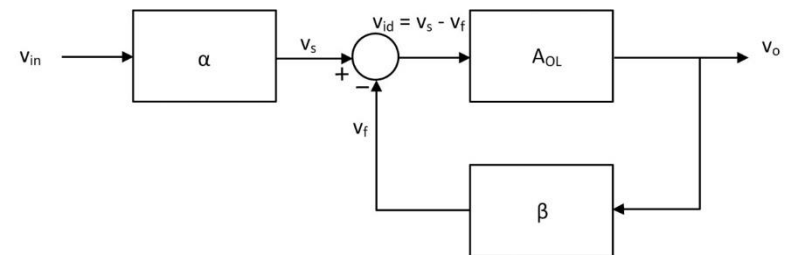

Bemærk  $\alpha = 1$  idet  $x_s$  betragtes som indgangssignal


$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \frac{1}{\beta} \Big|_{\beta A \rightarrow \infty}$$

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \frac{1}{\beta} \Big|_{\beta A \rightarrow \infty}$$

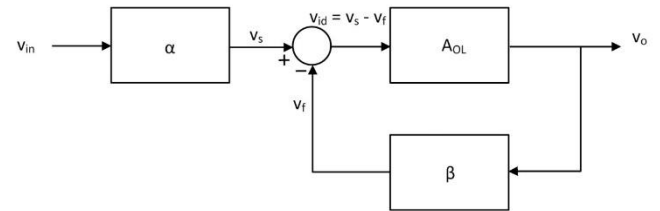

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \frac{1}{\beta} \Big|_{\beta A \rightarrow \infty}$$

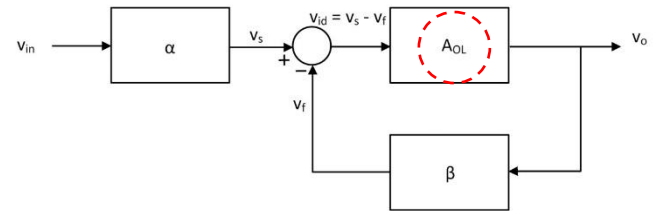
A: **Åbensløjfeforstærkningen** ( $A_{OL}$ )



$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \frac{1}{\beta} \Big|_{\beta A \rightarrow \infty}$$

$A$ : **Åbensløjfeforstærkningen** ( $A_{OL}$ )

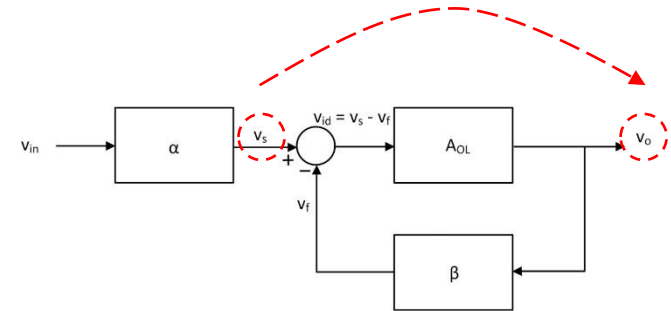$A_f$ : **Lukketsløjfeforstærkningen** ( $A_{CL}$ )






$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \frac{1}{\beta} \Big|_{\beta A \rightarrow \infty}$$

$A$ : **Åbensløjfeforstærkningen** ( $A_{OL}$ )

$A_f$ : **Lukketsløjfeforstærkningen** ( $A_{CL}$ )

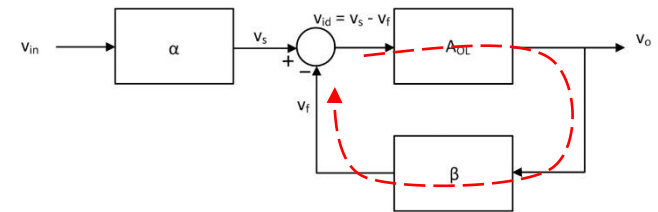$\beta A$ : **Sløjfeforstærkningen** ( $\beta A_{OL}$ )




$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \frac{1}{\beta} \Big|_{\beta A \rightarrow \infty}$$

$A$ : **Åbensløjfeforstærkningen** ( $A_{OL}$ )

$A_f$ : **Lukketsløjfeforstærkningen** ( $A_{CL}$ )

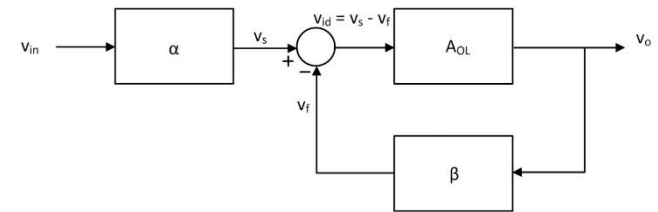$\beta A$  **Sløjfeforstærkningen** ( $\beta A_{OL}$ )



$A_f$  er hele kredsløbets  
performance set fra  
terminalerne udefra.

$$\beta A \gg 1$$

Lukketsløjfeforstærkningen  $A_f$  bliver uafhængig af  
åbensløjfeforstærkningen  $A$

$A$  afhænger ofte **markant** af den  
aktive komponents parametre ( $A_{OL}$ )

$\beta$  er typisk bestemt af **passive** komponenter:  $R$ ,  $C$ , etc.

$\beta$  er typisk bestemt af **passive** komponenter:  $R, C$ , etc.


Hvis:

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + \beta \cdot A} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta \cdot A}} \rightarrow \left. \frac{1}{\beta} \right|_{\beta A \rightarrow \infty}$$

...kan man udskifte den **aktive komponent** og opnå **uændret performance**, hvis blot...

$$\beta A \gg 1$$

# Feedback typer

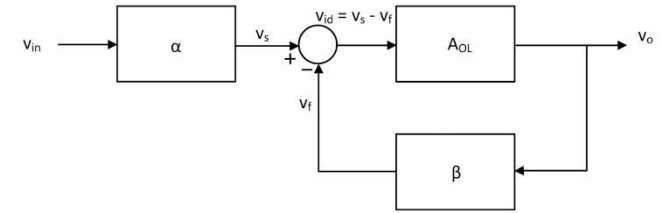


Hvordan feedback signalet **samples**



Spænding/strøm

# Feedback typer

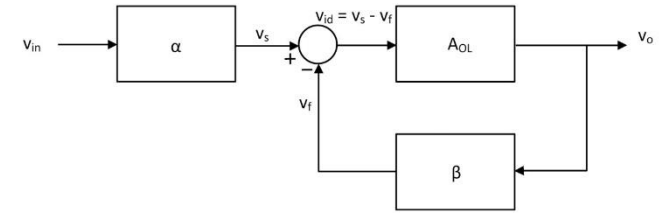


Hvordan feedback signalet **samples**


Spænding/strøm

Hvordan feedback signalet **føres tilbage**


Serie/parallel

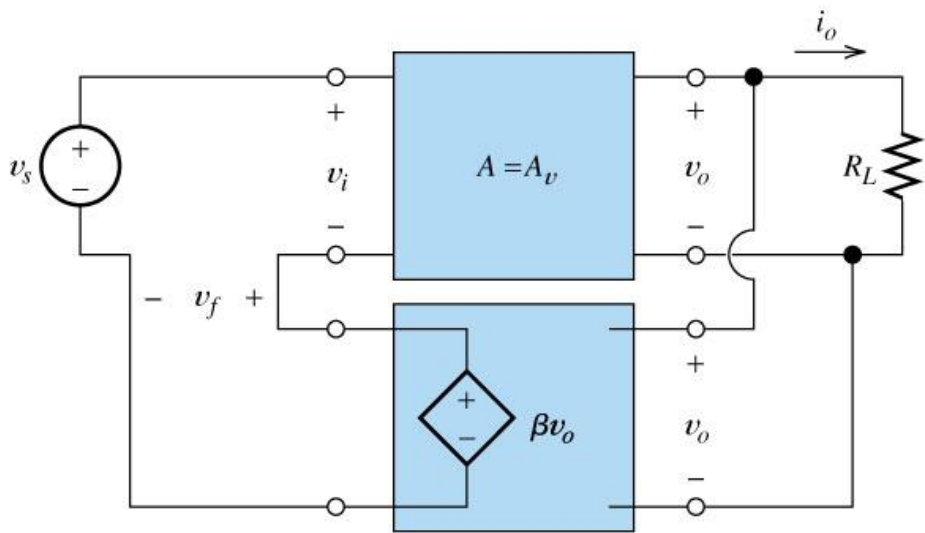


(a) Series voltage feedback

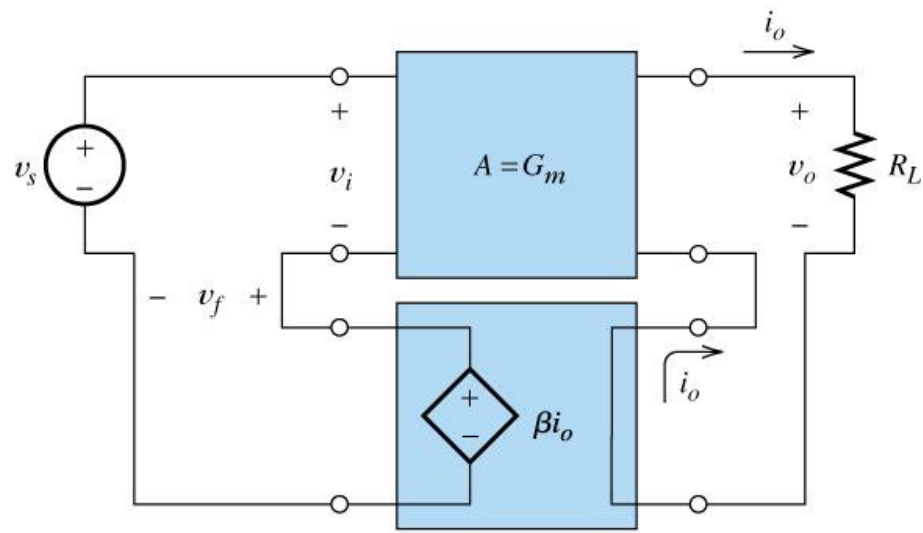

(b) Series current feedback

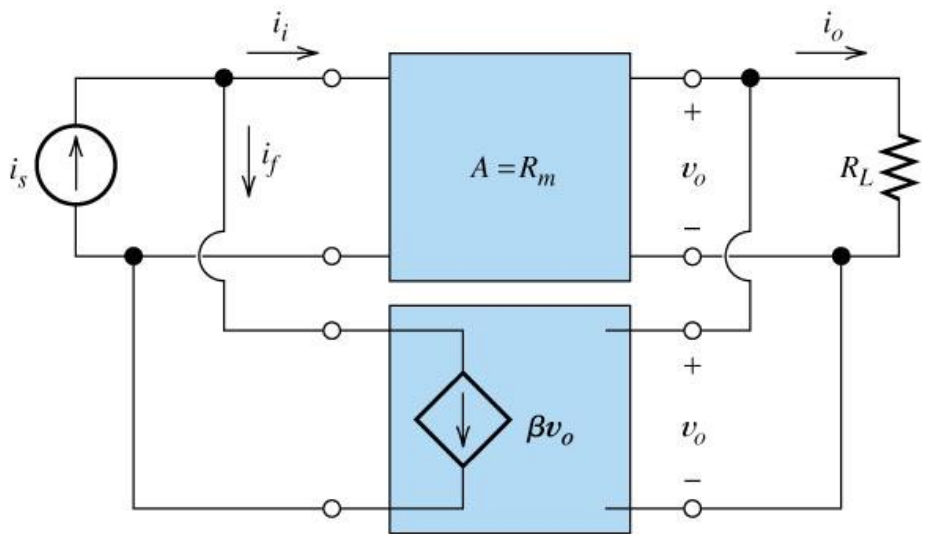

(c) Parallel voltage feedback

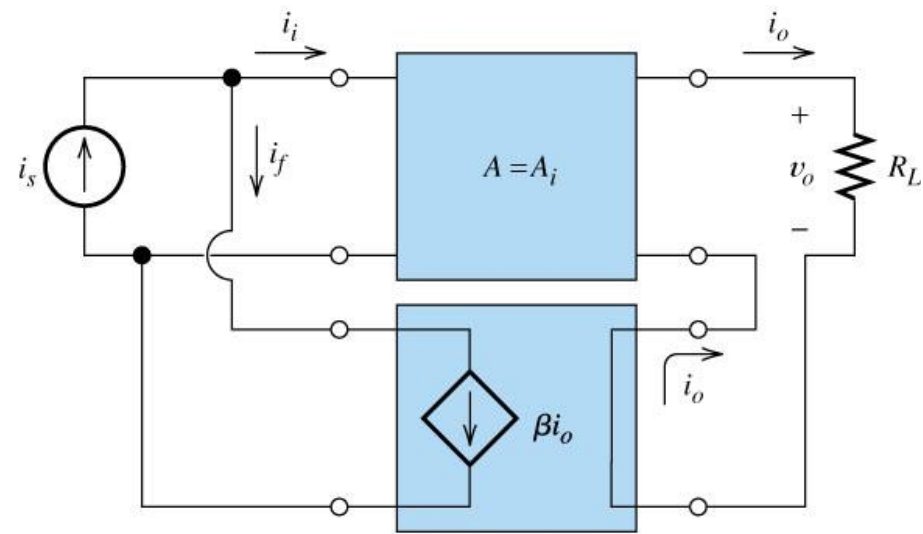


(d) Parallel current feedback

Figur 9.14
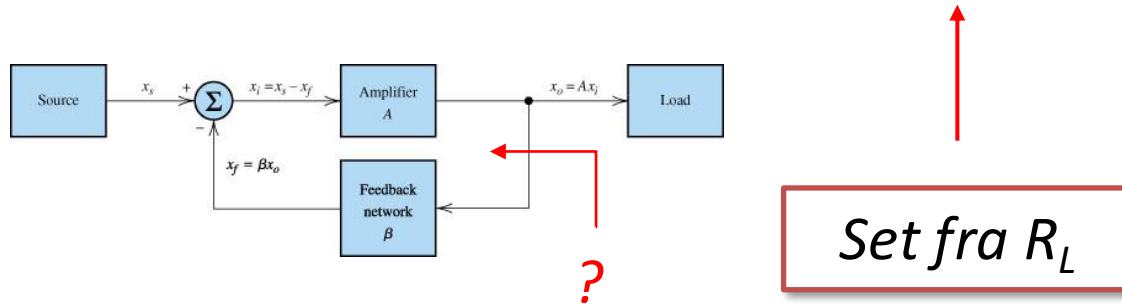
# Baggrund for valg af feedback type


Hvordan skal kredsløbet se ud som **kilde**?





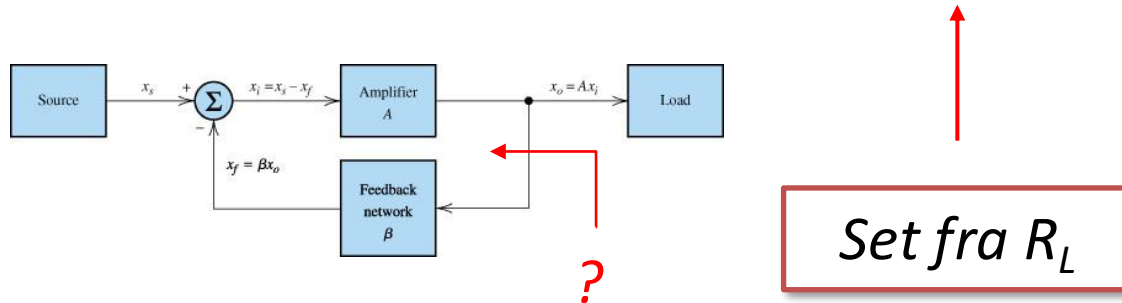
# Baggrund for valg af feedback type

Hvordan skal kredsløbet se ud som **kilde**?




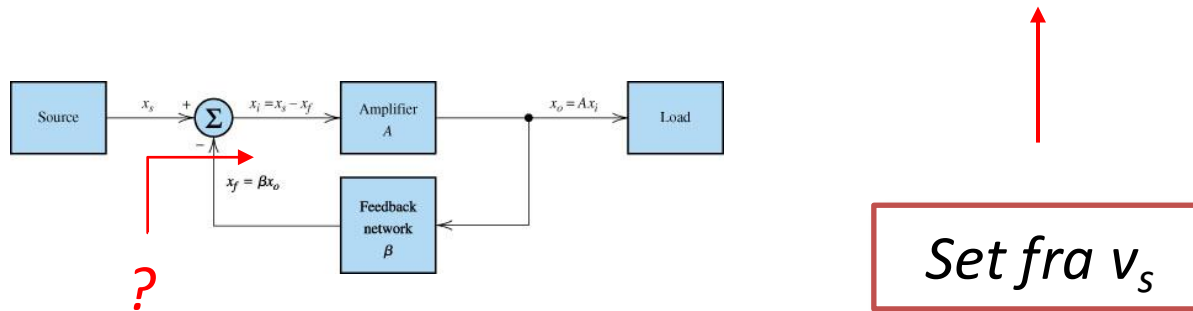Hvordan skal kredsløbet se ud som **belastning**?



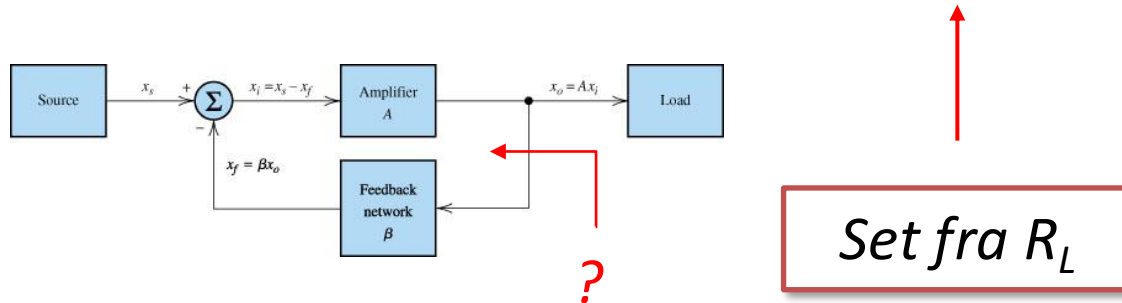
# Baggrund for valg af feedback type

Hvordan skal kredsløbet se ud som **kilde**?



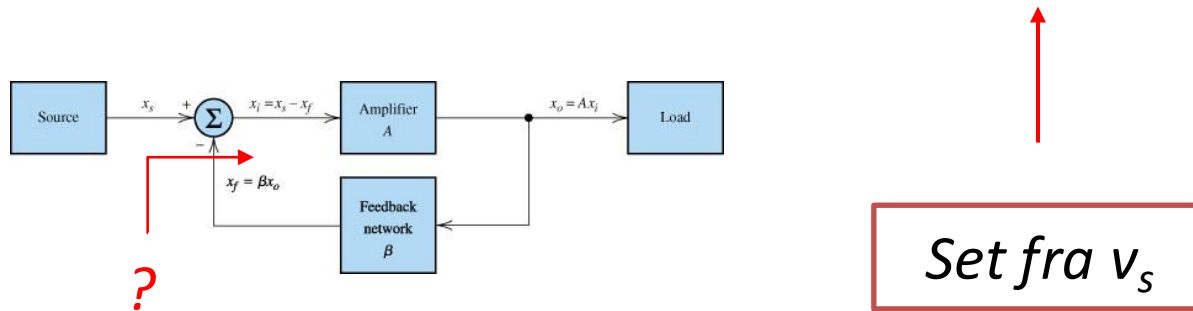Hvordan skal kredsløbet se ud som **belastning**?



Thevenin og Norton betragtninger  $\longrightarrow$

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

*Vær opmærksom på type af forstærkeren i reguleringsløjfen!*

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

$$R_{if} \rightarrow \infty$$

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.



**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

$$R_{if} \rightarrow 0 \Omega$$

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.



$$R_{of} \rightarrow 0 \Omega$$

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

$$R_{of} \rightarrow 0 \Omega$$

*Ideel spændingskilde*

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series <span style="border: 1px solid red; padding: 2px;">voltage</span>	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	<span style="border: 1px solid red; padding: 2px;"><math>\frac{R_o}{1 + \beta A_{voc}}</math></span>	Voltage
Series current	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	$R_o(1 + \beta G_{msc})$	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series <b>current</b>	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	<b><math>R_o(1 + \beta G_{msc})</math></b>	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.

$$R_{of} \rightarrow \infty$$

**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series <b>current</b>	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	<b><math>R_o(1 + \beta G_{msc})</math></b>	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.



$$R_{of} \rightarrow \infty$$

*Ideel strømkilde*


**Table 9.1.** Effects of Feedback<sup>a</sup>

Feedback Type	$x_s$	$x_o$	Gain Stabilized	Input Impedance	Output Impedance	Ideal Amplifier
Series voltage	$v_s$	$v_o$	$A_{vf} = \frac{A_v}{1 + A_v\beta}$	$R_i(1 + A_v\beta)$	$\frac{R_o}{1 + \beta A_{voc}}$	Voltage
Series <b>current</b>	$v_s$	$i_o$	$G_{mf} = \frac{G_m}{1 + G_m\beta}$	$R_i(1 + G_m\beta)$	<b><math>R_o(1 + \beta G_{msc})</math></b>	Transconductance
Parallel voltage	$i_s$	$v_o$	$R_{mf} = \frac{R_m}{1 + R_m\beta}$	$\frac{R_i}{1 + R_m\beta}$	$\frac{R_o}{1 + \beta R_{moc}}$	Transresistance
Parallel current	$i_s$	$i_o$	$A_{if} = \frac{A_i}{1 + A_i\beta}$	$\frac{R_i}{1 + A_i\beta}$	$R_o(1 + \beta A_{isc})$	Current

<sup>a</sup> Formulas given assume an ideal controlled source for the feedback network (as shown in Figure 9.14), zero source impedance for series feedback, and infinite source impedance for parallel feedback. Gains with subscripts sc and oc are for short-circuit and open-circuit loads, respectively. The gains  $A_v$ ,  $G_m$ ,  $R_m$ , and  $A_i$  are for the actual load.
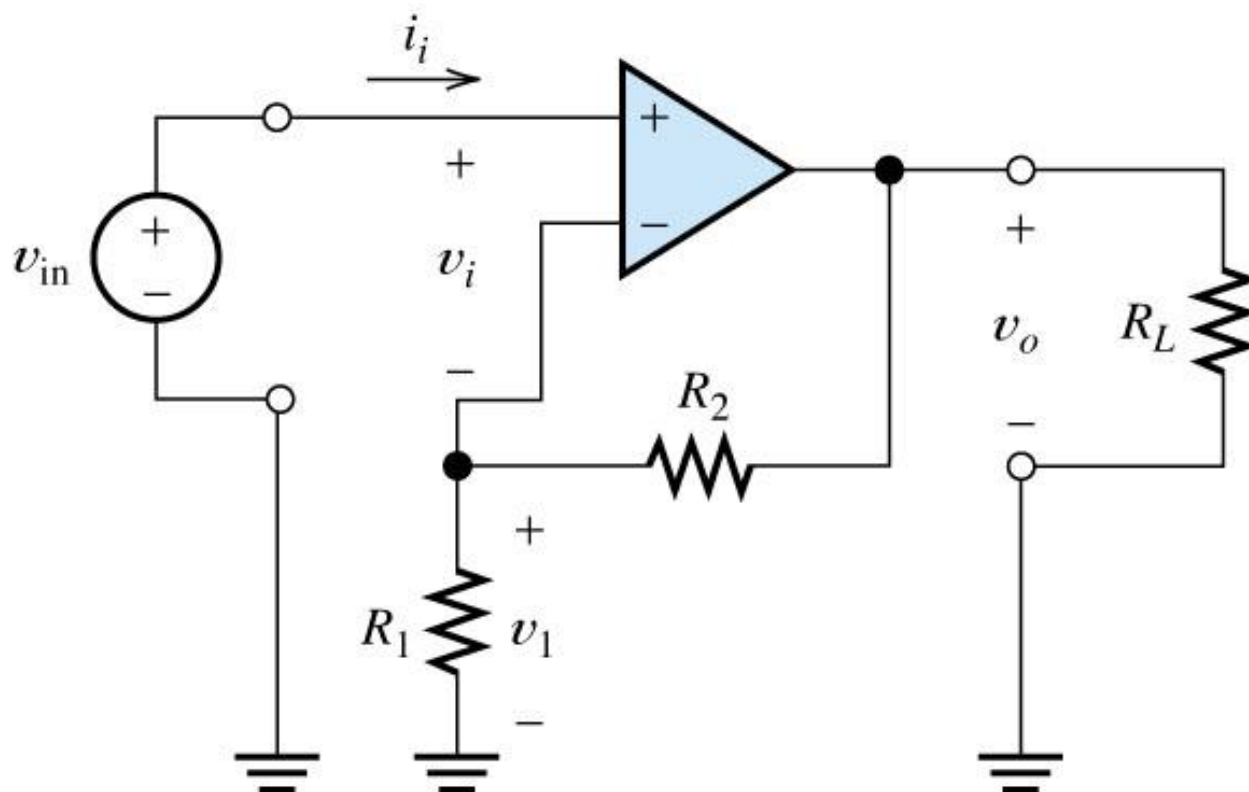
### Sp. 5 fra forberedelsen:

En ikke-inverterende forstærker som på figur 2.11 er bygget med  $R_1 = 10 \text{ k}\Omega$  og  $R_2 = 90 \text{ k}\Omega$ . Forstærkeren kan regnes ideel bortset fra en indgangsmodstand på  $R_{in} = 1 \text{ M}\Omega$  samt en endelig åbensløjfeforstærkning på  $A_{OL}$ .



Find bogstavudtryk og talværdi for  $\alpha$ ,  $\beta$  samt  $\frac{\alpha}{\beta}$ . Hvad bliver kravet til  $A_{OL}$  såfremt fejlen på lukketsløjfe forstærkningen  $A_v = \frac{v_o}{v_{in}}$  ikke må overstige 100 ppm?